

EECS2070 02 Exam 2_2

15:30 ~ 17:30, December 14, 2021

➤ Instructions

1. There are **one (1) design problem** in this exam, with the PDF specification of **four (4) pages** in total.
 - You also have the hardcopy of the first page to sign and hand back.
2. Download the ***.cpp** files from OJ. Change them to ***.zip** and decompress them. (Skip the *.h file, which the OJ system enforces to have.)
3. Submit each Verilog code to OJ **immediately** after it is done.
 - a. You have the responsibility to check if the submission is successful. The incorrect submission results in a zero score.
 - b. The module names should be **exam2_2**.
 - c. The first line of each Verilog code should be a comment with your student ID and name as follows:

```
// 107123456 王小明  
module exam2_2 (...
```
 - d. The **exam2_2.v** should be able to be compiled by Vivado, generating the bit file.
 - e. **The submission is due at 17:30!**
4. Please **take the OJ password slip with you** when leaving your seat. Do not litter!
5. The score will get deducted if you fail to follow the rules.
6. **Hand back this problem sheet with all the following items checked. Also, sign your name with your student ID.**

- ☐ I confirm that I read the instructions carefully and understand that my score will get deducted if failing to follow the rules.
- ☐ I confirm that I follow the naming rule of the modules. And the first line of each answer code shows my student ID and name.
- ☐ I confirm that all my answers were submitted successfully.
 - ✓ I've submitted the module **exam2_2** and the complete design in a single file. And that single file can be synthesized, generating the bit file.
 - ✓ I understand that the generated bit file will be scored. And the incorrect submission will result in a zero score.
- ☐ I hereby state that all my answers are done on my own.

ID: _____ Name: _____

➤ Design Problems


[100%] [FPGA Implementation]

1. Use the Verilog template **exam2_2.v** to implement a counter. DO NOT modify I/O signals of **exam2_2**.
2. The state machine is synchronous with the clock rate of 100MHz / 2^{25}
3. The seven-segment display is synchronous with the clock rate of 100MHz / 2^{15}
4. Your design should be reset **synchronously**.
5. Your design should change its value at the **positive edge** of each clock cycle.
6. Here is the table showing the function with the I/O connection:

Name	I/O	Pin	Description
clk	Input	W5	100MHz clock signal
rst	Input	BTNC	Active-high reset
en	Input	BTNR	Control the states
PS2_CLK	Inout	C17	Signal used for the keyboard
PS2_DATA	Inout	B17	Signal used for the keyboard
DIGIT [3:0]	Output	4-Digits Pin	Display counter
DISPLAY [6:0]	Output	7-Segment Pin	Display counter
led [15:0]	Output	16-LEDs	Display state

7. Please refer to the demo video (**exam2_2_DEMO.mp4**) for further details.

 8. The design concept to help you understand:



9. Function description

- (1) LED is used to indicate which state it is.
- (2) Implement a ticket machine.
- (3) There are three states: **AMOUNT**, **DEPOSIT**, and **CHANGE**.

● AMOUNT

Everything should be initiated in the beginning. **The number of tickets is one, initially.** The price for ticket is \$15. Choose the amount of tickets wanting to buy with keyboard “numpad 1”, “numpad 2” and “numpad 3”, and show it on the rightmost 7-segment digit.


- (a) State transition:

After pressing the en button, change to the **DEPOSIT** state.

- (b) LED

led [12:15] (P3~L1) are on; others are off.

- (c) Seven-segments

 

● DEPOSIT

The two rightmost 7-segment digits will show the **Money** you deposit. When keyboard “numpad 0” (\$10) or keyboard “numpad 5” (\$5) is pressed, the corresponding amount of money will be deposited.

The two leftmost 7-segment digits will show the **Price** you need to pay (the amount multiply the ticket price) **only when you press and hold the Space key**. Otherwise, show “00”.

****Note:** assume that the number key and Space key will not be pressed at the same time.


- (a) State transition

When the **Money** you deposit is equal to or greater than the **Price** you need to pay, change to the **CHANGE** mode.


- (b) LED

led [8:11] (V13~U3) are on, others are off.

- (c) Seven-segment display:

 

Or

 

● CHANGE

The two rightmost 7-segment digits will show the **Change** to be returned. **Change** Start from the remaining money (**Money - Price**), and it will be decreased by \$1 (to simulate dropping a \$1 coin) with the frequency of $\text{clk} / (2^{25})$.

****Note:** when the **Change** decreases to zero in the end, you still need to show "0000" for a clock.


(a) State transition

After showing "0000", return to the **AMOUNT** mode.

(b) LED

led [4:7] (W18~V14) are on, others are off.

(c) Seven-segment display:

 

10. Refer to the XDC constraint file (**exam2_2.xdc**) for the pin connection. Also, DO NOT modify the constraint file. Otherwise, your design will fail the synthesis then get a ZERO score.

11. There are already several modules in the template, including the clock divider, seven-segments, debounce, one-pulse, and KeyboardDecoder modules. You can modify them if necessary.

NOTE: The submitted exam2_2.v should be **self-contained**. That is, you must include **all the modules** you need in the single file and submit it, or you will get a 5 points penalty.

12. Grading

Function	Score
LED	10%
AMOUNT	20%
Money in DEPOSIT state	25%
Price in DEPOSIT state	20%
CHANGE	25%

Happy Designing and Good luck!